

Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	09/ 10 /2023	Batch No:	D-2
Faculty Name:	Ruchira Jadhav	Roll No:	16010122323
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 7 Title: Asynchronous Counter

Aim and Objective of the Experiment:

To design and implement 3 bit Asynchronous up counter using JK Flip Flop

COs to be achieved:


CO3: Design synchronous and asynchronous sequential circuits.

Tools used:


Trainer kits

Theory:

 Circuit diagram of 3 bit Asynchronous Up counter using JK FF (IC 7476)



Pin diagram of JK FF (IC 7476)

 

7476

Implementation Details

Procedure

- 1) Locate IC 7476 JK FF on Digital trainer kit
- 2) Apply various inputs to appropriate pins as per the circuit diagram of the 3 bit Asynchronous up counter with reference to the pin configuration of the IC.
- 3) Make sure of Reset and Clear Pins connections with reference to data sheet information.
- 4) Connect a pulsar switch to the clock input.
- 5) Verify the working and prepare a truth table.

Post Lab Subjective/Objective type Questions:

1. How JK FF need to be configured to use for counter operation?

Ans) **Common types of counters include:**

Up Counters: These count upwards from a starting point to an ending point. JK Flip-Flops in this configuration should be connected to toggle when the count reaches a specific value.

Down Counters: These count downwards from a starting point to an ending point. JK Flip-Flops in this configuration should be connected to toggle when the count reaches a specific value.

Binary Counters: These use a series of JK Flip-Flops to count in binary. Each Flip-Flop represents a different bit in the binary number.

Ring Counters: In a ring counter, the output of one Flip-Flop is connected to the input of the next one, creating a "ring" of Flip-Flops that cycle through a specific sequence.

2. What changes are required to use the same counter as 3 bit asynchronous down counter?

Ans) **the steps to modify a counter into a 3-bit asynchronous down counter:**

Change the initial state: For an up counter, the initial state is typically 000. In a down counter, the initial state should be set to the highest count value, which is 111 for a 3-bit counter.

Change the count sequence: In an up counter, the Flip-Flops are usually configured to increment the count on clock pulses. In a down counter, they should decrement the count when a clock pulse is received.

Update the JK Flip-Flop configurations: To create a 3-bit asynchronous down counter, set up the JK Flip-Flops as follows:

For the first Flip-Flop (LSB), configure J=0 and K=1. This means it toggles (Q flips) on every clock pulse.


For the second Flip-Flop, connect its clock input to the output of the first Flip-Flop and configure J=0 and K=1. This Flip-Flop toggles on the falling edge of the clock signal,

creating a binary "10" sequence.

For the third Flip-Flop (MSB), connect its clock input to the output of the second Flip-Flop and configure $J=0$ and $K=1$. This Flip-Flop toggles on the falling edge of the second Flip-Flop's output, creating a binary "100" sequence.

Clock signal: Ensure that the clock signal is provided appropriately to all Flip-Flops, and that it should trigger them on the falling edge (because you are counting down).

 3. Draw the timing diagram of 3 bit Asynchronous up counter.



Ans)

4. What is mod n concept used in counters?

Ans) **The "mod n" concept in counters refers to the counting range or the maximum count value that a counter can reach before it resets back to zero (or another predefined starting value). It's a fundamental concept in digital electronics and is often used to design counters for specific applications.**

In the context of counters, "mod n" means that the counter will count from 0 to n-1 before resetting. Here's a breakdown of how it works:

Modulus (n): This represents the counting range of the counter. For example, if you have a "mod 10" counter, it means the counter will count from 0 to 9 before resetting. In binary, a "mod 10" counter counts from 0000 to 1001 (0 to 9 in decimal).

Reset to 0: When the counter reaches its maximum count value (n-1), it resets back to 0. This reset can be triggered by a clock signal or some other control signal.

5. For Mod-5 counter how many JK FFs are required?

Ans) **3**

Conclusion:

In this experiment, we learned to design and implement 3 bit Asynchronous up counter using JK Flip Flop

Signature of faculty in-charge with Date: