



K. J. Somaiya College of Engineering, Mumbai-77

Experiment / Assignment / Tutorial No. 4

Grade: AA / AB / BB / BC / CC / CD / DD

Signature of the Staff In-charge with date

Batch: D2

Roll No.: 16010122323

Experiment / assignment / tutorial No.: 4

Title: 4 bit Magnitude Comparator

Objective: Design a 2-bit comparator using logic gates and verify 4-bit magnitude comparator using IC 7485

Expected Outcome of Experiment:

CO2: Use different minimization technique and solve combinational circuits, synchronous & asynchronous sequential circuits.

Books/ Journals/ Websites referred:


- VLab Link: <http://vlabs.iitb.ac.in/vlabs-dev/labs/dldesignlab/experimentlist.html>
- R. P. Jain, "Modern Digital Electronics", Tata McGraw Hill
- M. Morris Mano, "Digital Logic & computer Design", PHI
- http://elnsite.teilam.gr/ebooks/digital_design/lab/dataSheets_page/7485.pdf

Pre Lab/ Prior Concepts:

The comparison of two numbers is an operator that determines one number is greater than, less

K. J. Somaiya College of Engineering, Mumbai-77

 than (or) equal to the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitude. The outcome of the comparator is specified by three binary variables that indicate whether $A > B$, $A = B$ (or) $A < B$.



Two Bit Magnitude Comparator Implementation Details:

Truth Table

A1	A0	B1	B0	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0



K. J. Somaiya College of Engineering, Mumbai-77

From the Truth Table:


$$(A < B) = A1'B1 + A0'B1B0 + A1'A0'B0$$

$$(A = B) = A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0'$$

$$(A > B) = A1B1' + A0B1'B0' + A1A0B0'$$

K. J. Somaiya College of Engineering, Mumbai-77

Logic Diagram of 2 bit Comparator

 

K. J. Somaiya College of Engineering, Mumbai-77


Comparing Table:

comparing inputs				comparing IP			output		
A_3, B_3	A_2, B_2	A_1, B_1	A_0, B_0	$A > B$	$A < B$	$A = B$	$A > B$	$A < B$	$A = B$
$A_3 > B_3$	X	X	X	X	X	X	H	L	L
$A_3 < B_3$	X	X	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 > B_2$	X	X	X	X	X	H	L	L
$A_3 = B_3$	$A_2 < B_2$	X	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	X	X	X	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	X	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	X	X	X	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	X	X	X	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	L	L	H	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	H	L	L	H	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	H	L	L	H
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	X	X	H	L	L	H
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	H	H	L	L	L	L
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	L	H	H	L

K. J. Somaiya College of Engineering, Mumbai-77

Four Bit Magnitude Comparator Implementation Details

Pin Diagram of IC 7485

 

K. J. Somaiya College of Engineering, Mumbai-77

Conclusion: In this experiment, we learned to design a 2-bit comparator using logic gates and verify 4-bit magnitude comparator using IC 7485

Post-Lab Descriptive Questions

1. Design a 1-bit magnitude comparator using logic gates.

