



Course Name:	Digital Design Laboratory	Semester:	III
Date of Performance:	___ / ___ / _____	Batch No:	D2
Faculty Name:		Roll No:	1601012232 3
Faculty Sign & Date:		Grade/Marks:	___/25

Experiment No: 2

Title: Binary Adders and Subtractors

Aim and Objective of the Experiment:

To implement half and full adder-subtractor using gates and IC 7483

COs to be achieved:

CO2: Use different minimization technique and solve combinational circuits.

Tools used:

Trainer kits

Theory:

Adder: The addition of two binary digits is the most basic operation performed by the digital computer. There are two types of adder:

- Half adder
- Full adder

Half Adder: Half adder is a combinational logic circuit with two inputs and two outputs. It is the basic building block for the addition of two single-bit numbers.

Full adder: A half adder has a provision not to add a carry coming from the lower order bits when multi-bit addition is performed. for this purpose, a third input terminal is added and this circuit is to add A, B, and C where A and B are the nth order bits of the number A and B respectively and C is the carry generated from the addition of (n-1) order bits. This circuit is referred to as full adder.

Subtractor: Subtraction of two binary digits is one of the most basic operations performed by digital computer .there are two types of subtractors:

- Half subtractor

- Full subtractor

Half subtractor: Logic circuit for the subtraction of B from A where A,B are 1 bit numbers is referred to as half subtract or .the subtract or process has two input and difference and borrow are the two outputs.

Full subtractor: As in the case of the addition using logic gates, a full subtractor is made by combining two half-sub tractors and an additional OR-gate. A full subtractor has the borrow in capability (denoted as BOR_{IN}) and so allows cascading which results in the possibility of multi-bit subtraction.

IC 7483

For subtraction of one binary number from another, we do so by adding 2's complement of the former to the latter number using a full adder circuit.

IC 7483 is a 16 pin, 4-bit full adder. This IC has a provision to add the carry output to transfer and end around carry output using Co and C4 respectively.


2's complement: 2's complement of any binary no. can be obtained by adding 1 in 1's complement of that no.

e.g. 2's complement of $+(10)_{10} = 1010$ is


$$\begin{array}{r} \text{1C of } 1010 \qquad 0101 \\ + \qquad \qquad \qquad 1 \\ \hline \text{-(10)}_{10} \qquad \qquad 0110 \end{array}$$

In 2's complement subtraction using IC 7483, we are representing negative number in 2's complement form and then adding it with 1st number.

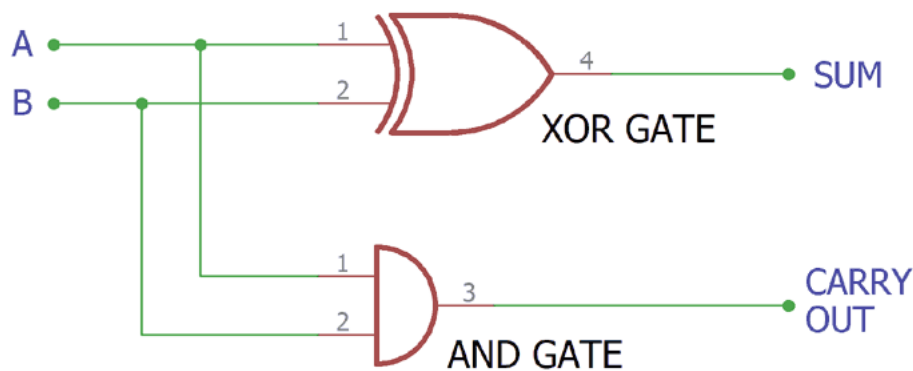Implementation Details: Half Adder Block Diagram



Half Adder Circuit

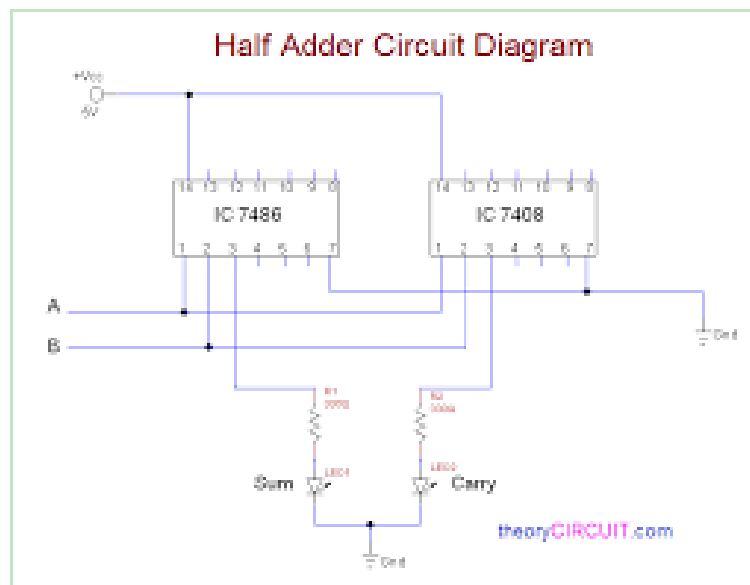

Truth Table for Half Adder

Inputs		Outputs	
A	B	A	B
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

From the truth table (with steps):

$0+0=0$ no carry

$0+1=1$ no carry


$1+0=1$ no carry

$1+1=2=1\ 0=1$ carry, sum=0


Sum=A xor B

Carry=A and B

Full Adder Block Diagram

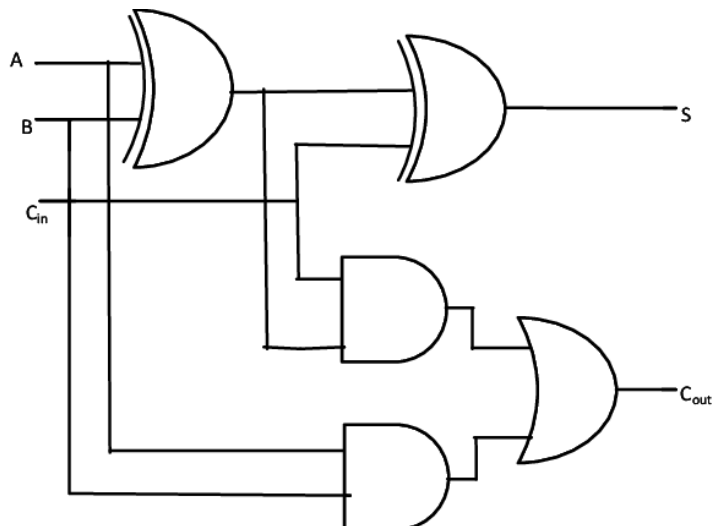

Full Adder Circuit

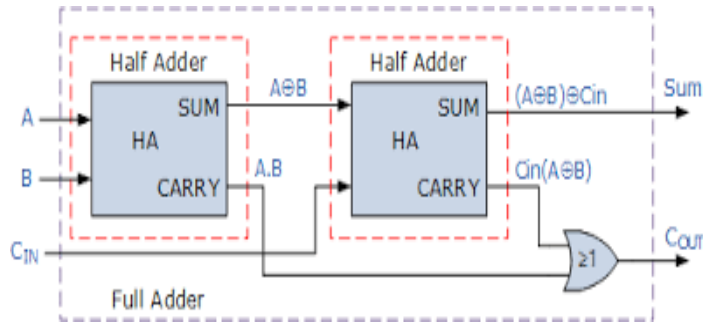

Truth Table for Full Adder

Inputs			Outputs	
A	B	C – IN	Sum	C – Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

From the truth table (with steps):

$$0+0+0=0$$

$$0+0+1=1$$

$$0+1+1=2 \text{ 1 carry+0 sum}$$

$$0+1+0=1$$

$$1+1+0=2 \text{ 1 carry+0 sum}$$

$$1+1+1=3 \text{ 1 carry+1 sum}$$


$$1+0+0=1$$

$$1+0+1=2 \text{ 1 carry+0 sum}$$


$$\text{Sum} = A'B'C\text{-IN} + A'B C\text{-IN} + AB'C\text{-IN}' + AB C\text{-IN}$$

$$\text{C-out} = A'B C\text{-IN} + AB'C\text{-IN} + AB C\text{-IN}' + AB C\text{-IN}$$

Half Subtractor Block Diagram

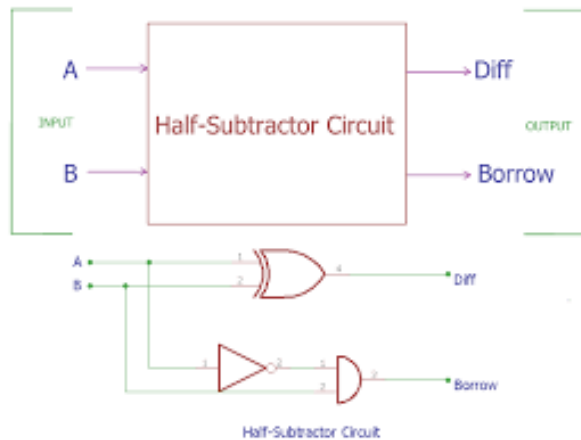


Half Subtractor Circuit

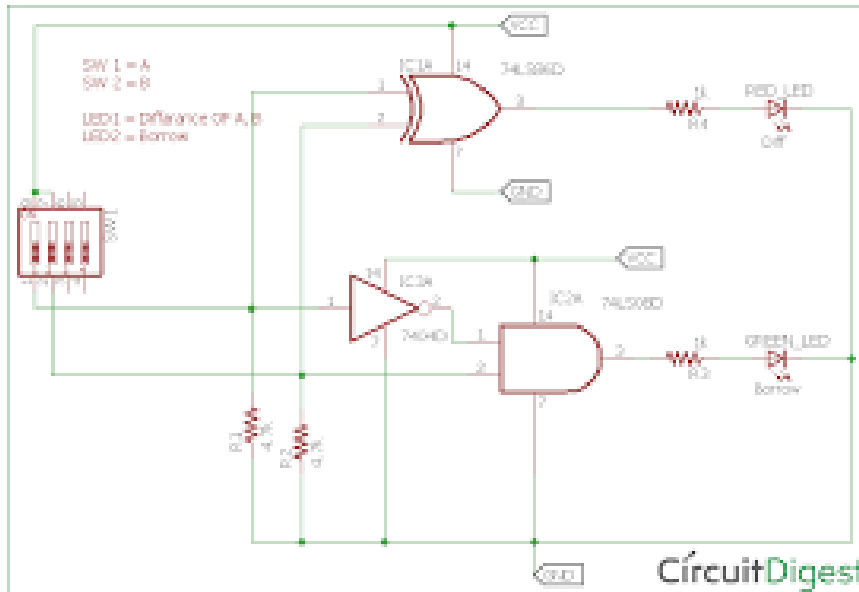

Truth Table for Half Subtractor

A	B	DIFFERENCE(D)	BORROW(Bo)
1	0	1	0
1	1	0	0
0	0	0	0
0	1	0	1

Full Subtractor Circuit

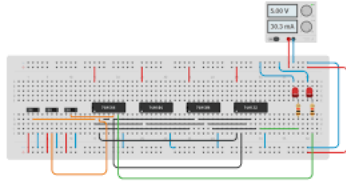

Truth Table for Full subtractor

A	B	BIN	D	BOROUT
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From the truth table (with steps):

$$\text{Bout} = A'B_{in} + A'B + B B_{in}$$

$$\text{Diff} = B_{in}(A'B' + AB) + B_{in}'(AB' + A'B)$$

Example:

1) $7_{10} - 2_{10} = 5_{10}$

7 0111

2 0010

1'C of 2 1101

+ 1


2'C of 2 1110

1110

0111 + 1110 1
 0101

Pin Diagram IC7483

Adder

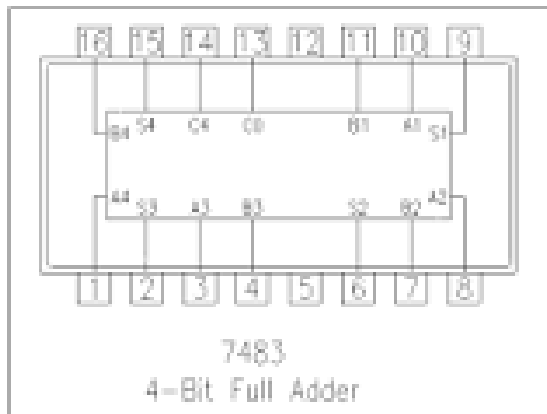

Subtractor




Implementation Details

Procedure:

- 1) Locate the IC 7483 and 4-not gates block on trainer kit.
- 2) Connect 1st input no. to A4-A1 input slot and 2nd (negative) no. to B4-B1 through 4-not gates (1C of 2nd no.)
- 3) Connect high input to Co so that it will get added with 1C of 2nd no. to get 2C.
- 4) Connect 4-bit output to the output indicators.
- 5) Switch ON the power supply and monitor the output for various input combinations.

Post Lab Subjective/Objective type Questions:

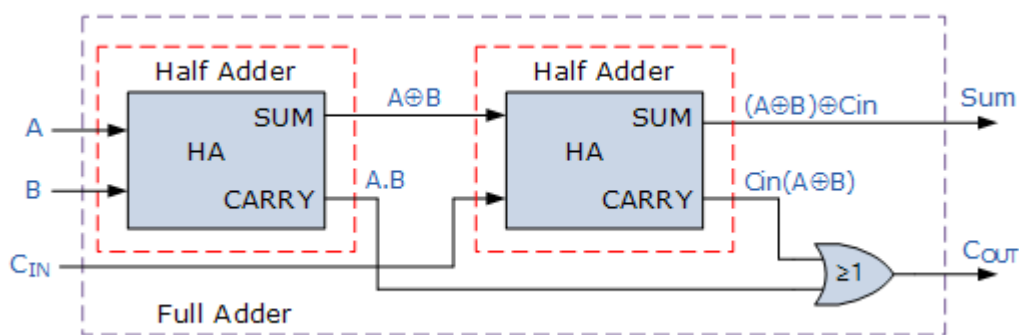1. Design a full adder using two half adders.



2. Perform the following Binary subtraction with the help of appropriate ICs:

- 6-4
- 5-8
- 7-9

(02)

(a) 6-4

(i) $6 = 0110$
 $4 = 0100$

(ii) Performing binary subtraction

(iii) Ans: 0010

(b) 5-8

(i) $5 = 0101$
 $8 = 1000$

(ii) Performing binary subtraction

$$\begin{array}{r} 0101 \quad (5) \\ - 1000 \quad (8) \\ \hline 1101 \quad (-3) \end{array}$$

(c) 7-9

~~Step 1~~

(i) $7 = 0111$ $9 = 1001$

(ii) Performing binary subtraction

$$\begin{array}{r} 0111 \quad (7) \\ - 1001 \quad (9) \\ \hline 1110 \quad (-2) \end{array}$$



Conclusion:

Thus we have made use of half adder, full adder ,half subtractor and full subtractor and understood the implementation and working.

Signature of faculty in-charge with Date: