

**Batch: D-2 Roll No.: 16010122323 Experiment / assignment / tutorial No.: 8**

**Title: 4:1 Mux in VHDL**

**Objective:** Design of 3-bit asynchronous counter using JK flip flop in VHDL

**Expected Outcome of Experiment:**

**CO2:** Use different minimization technique and solve combinational circuits, synchronous & asynchronous sequential circuits.

**CO4:** Implement digital networks using VHDL

**Books/ Journals/ Websites referred:**

- VLab Links: <http://vlabs.iitb.ac.in/vlabs-dev/labs/dldesignlab/experimentlist.html>
- R. P. Jain, "Modern Digital Electronics", Tata McGraw Hill
- M. Morris Mano, "Digital Logic & computer Design", PHI
- <https://wiki.engr.illinois.edu/download/attachments/84770821/08-Multiplexers.pdf?version=2&modificationDate=1285128827000>

**Pre Lab/ Prior Concepts:**

**Multiplexer:** Multiplexer is a special type of combinational circuit. It is a digital circuit which selects one of the  $n$  data inputs and routes it to the output. The selection of one of the  $n$  inputs is done by the select lines. To select  $n$  inputs, we require  $m$  select lines, such that  $2^m = n$ . Depending on the digital code applied at the select inputs, one out of the  $n$  data sources is selected and transmitted to a single output. It is called as the strobe or enable input which is useful for cascading. It is generally on active low terminal that means it will perform the required operation when it is low. The multiplexer act like a digitally controlled single pole, multiple way switches. The output gets connected to only one input at a time. In most of the electronic system the digital data is available on more than one line. It is necessary to route the data over a single line, under such circumstances input at a time.

**Types of Multiplexers:**

1. 2:1 Multiplexer
2. 4:1 Multiplexer
3. 8:1 Multiplexer
4. 16:1 Multiplexer
5. 32:1 Multiplexer

**Implementation Details of 4:1 MUX**

```
library IEEE;
use IEEE.std_logic_1164.all;
use
    IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;
entity Mux_2_4 is
    port(
        a,b,c,d: in
            std_logic;
        --sel : in integer range
        0 to 3; --when we use if
        then statement.
        sel: in std_logic_vector
        (1 downto 0); --when we use
        when statement.
        z: out std_logic );
end Mux_2_4;
architecture Mux_2_4_arch of
    Mux_2_4 is
begin
    --process (a,b,c,d,sel)
    --begin


        z<=a when
    sel= "00"
        else b when
    sel= "01"
        else c when
    sel="10"
        else d when
    sel="11";
        --if (sel = 0) then z<=a;
        --elsif (sel=1)
    then z<=b;
        --elsif (sel=2)
    then z<=c;
        --elsif (sel=3)
    then z<=d;
        --end if;
    --end process;
end Mux_2_4_arch;
library IEEE;
use IEEE.std_logic_1164.all;
use
    IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;
entity Mux_2_4_tb is
end Mux_2_4_tb;
architecture Mux_2_4_arch_tb
    of Mux_2_4_tb is
component Mux_2_4 is
    port(
        a,b,c,d: in std_logic;
```

```

    sel:in std_logic_vector
    (1 downto 0);
    z: out std_logic
    );
end component;
signal      a1,c1:
    std_logic := '0';
signal      b1,d1:
    std_logic := '1';
signal      z1:
    std_logic;
signal sell :
    std_logic_vector (1 downto
    0) :="00";
begin
    u1: Mux_2_4 port
    map(a1,b1,c1,d1,sell,z1);
    process
        begin
            for i in 0 to
3 loop
                sell<=
sell+1;
                wait for
10ns;
            end loop;
        end process;
    end architecture;

```

### Output:

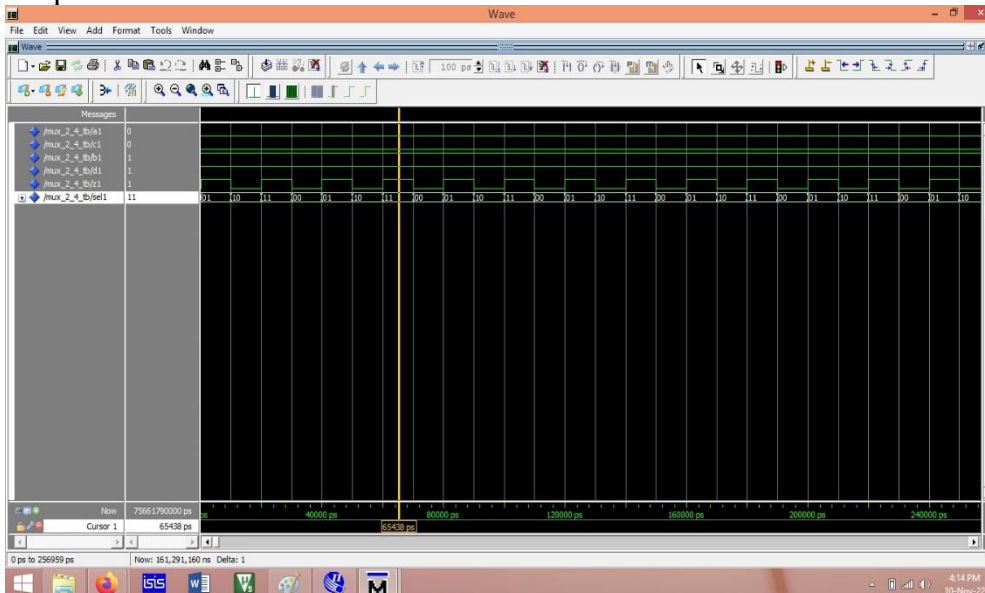

**Conclusion:** VHDL program for basic logic gates has been run and simulation obtained as required.

### Post Lab Descriptive Questions

#### 1. Application Mux?

Multiplexer are used in various fields where multiple data need to be transmitted using a single line.

Following is some of the applications of multiplexers –

- **Communication System** – Communication system is a set of system that enable communication like transmission system, relay and tributary station, and communication network. The efficiency of communication system can be increased considerably using multiplexer. Multiplexer allow the process of transmitting different type of data such as audio, video at the same time using a single transmission line.
- **Telephone Network** – In telephone network, multiple audio signals are integrated on a single line for transmission with the help of multiplexers. In this way, multiple audio signals can be isolated and eventually, the desired audio signals reach the intended recipients.
- **Computer Memory** – Multiplexers are used to implement huge amount of memory into the computer, at the same time reduces the number of copper lines required to connect the memory to other parts of the computer circuit.
- **Transmission from the Computer System of a Satellite** – Multiplexer can be used for the transmission of data signals from the computer system of a satellite or spacecraft to the ground system using the GPS (Global Positioning System) satellites.

This is just an introduction to the concept of Multiplexer. To learn more about Multiplexers, read this [Multiplexer \(MUX\) and Multiplexing tutorial](#)